

6.302 Feedback Systems

Recitation 24: Feedback Applications


Prof. Joel L. Dawson

We've been talking about how feedback is used successfully in countless different applications. We've said before, and I repeat here, it is astounding that the same feedback theory that helps stabilize an inverted pendulum helps us control op-amps. Or motors. Or magnetic levitation systems. The list goes on and on.

We're going to explore a couple more applications. But before we do, our traditional class exercise.

CLASS EXERCISE

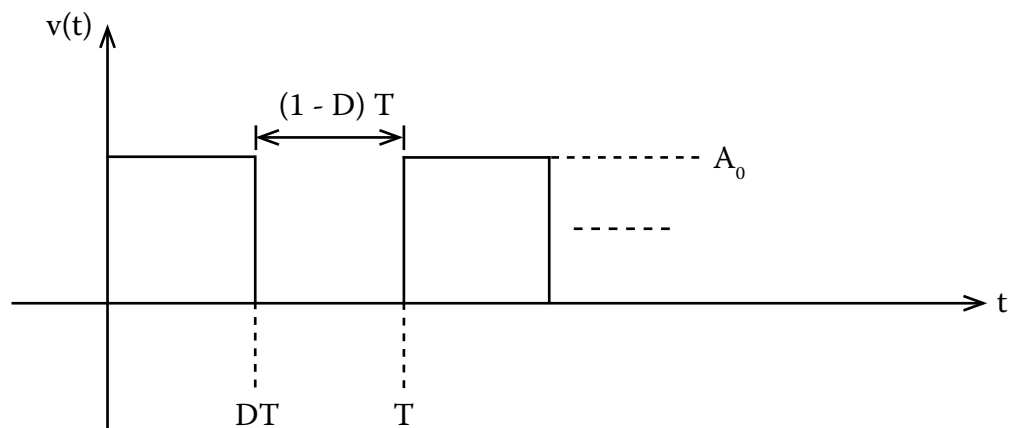Consider the following voltage wave form:



$$0 \leq D \leq 1$$

Compute the average, or DC, value of the waveform.

6.302 Feedback Systems


Recitation 24: Feedback Applications

Prof. Joel L. Dawson

In the waveform that you just analyzed, the parameter “D” is called the duty cycle. Modulating, or changing, the duty cycle in order to achieve a certain DC value is a common control technique. It is called pulse width modulation, or PWM.

One of the places PWM is useful is in voltage conversion. Often on a battery-powered device like a cellular phone, different parts of the system require different supply voltages. How might we solve this problem?

One way

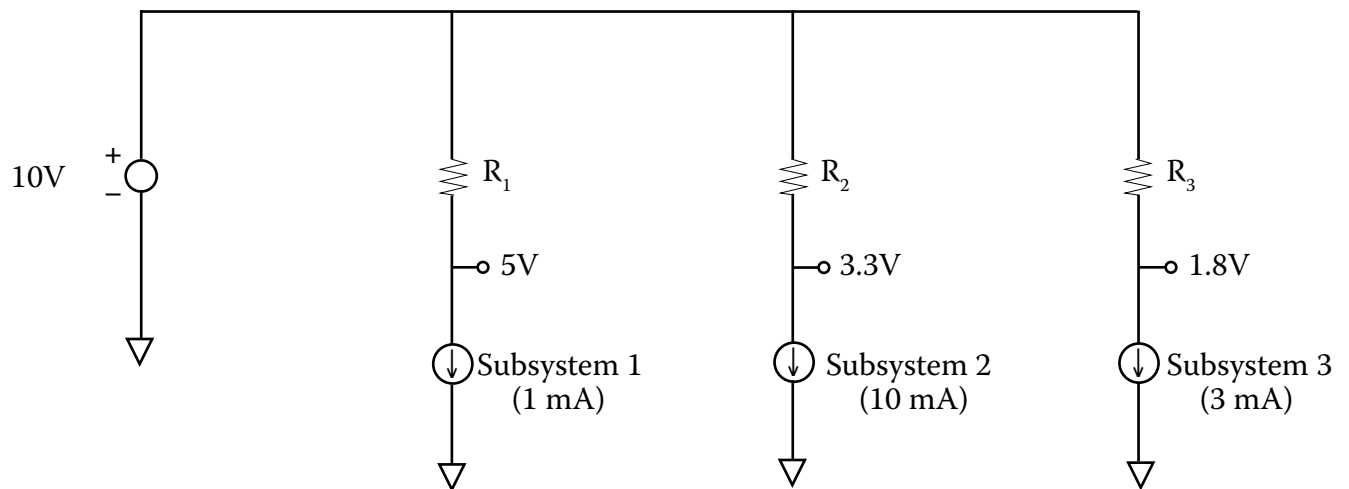

$$\begin{aligned} \text{Total power draw: } & 14 \text{ mA} \times 10\text{V} = 140\text{mW} \\ \text{Total power lost in resistors: } & (10\text{V} - 5\text{V}) \cdot 1\text{mA} \\ & (10\text{V} - 3.3\text{V}) \cdot 10\text{mA} \\ & + (10\text{V} - 1.8\text{V}) \cdot 3\text{mA} \\ & \underline{\hspace{1.5cm}} \\ & 96.6\text{mW} \end{aligned}$$

70% of power lost in voltage conversion.

UNACCEPTABLE.


6.302 Feedback Systems

Recitation 24: Feedback Applications

Prof. Joel L. Dawson

How can we do better? Not clear at this point, but a good start might be using components that are purely lossless.

Inductors:

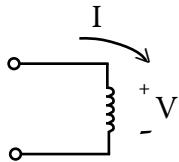


$$\begin{aligned} V &= IZ \\ &= Ij\omega L \\ &= I\omega L e^{j\pi/2} \end{aligned}$$

$$\begin{aligned} \langle P \rangle &= \frac{1}{2} \operatorname{Re} \{VI^*\} = \frac{1}{2} \operatorname{Re} \{I^2 \omega L e^{j\pi/2}\} \\ &= \frac{1}{2} I^2 \omega L \operatorname{Re} \{\cos 90^\circ + j\sin 90^\circ\} \\ &= 0 \end{aligned}$$



Inductors might help.

Capacitors:

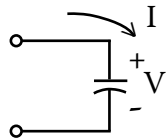

$$\begin{aligned} V &= I \cdot \frac{-j}{\omega C} \\ &= \frac{I}{\omega C} e^{-j\pi/2} \end{aligned}$$

$$\begin{aligned} \langle P \rangle &= \frac{1}{2} \operatorname{Re} \{VI^*\} = \frac{1}{2} \operatorname{Re} \{VI^*\} \\ &= \frac{1}{2} \operatorname{Re} \left\{ \frac{I^2}{\omega C} e^{-j\pi/2} \right\} \\ &= \frac{1}{2} \frac{I^2}{\omega C} \operatorname{Re} \{\cos 90^\circ - j\sin 90^\circ\} \\ &= 0 \end{aligned}$$




Capacitors might help.

6.302 Feedback Systems

Recitation 24: Feedback Applications
 Prof. Joel L. Dawson


Perfect Switches

When switch is OPEN:

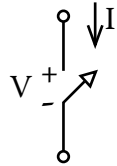

$I = 0$, V can be anything, $\Rightarrow I \cdot V = 0$ always.

When switch is CLOSED:


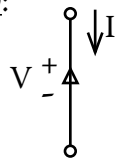


I can be anything, $V = 0 \Rightarrow I \cdot V = 0$ always



Switches might help.

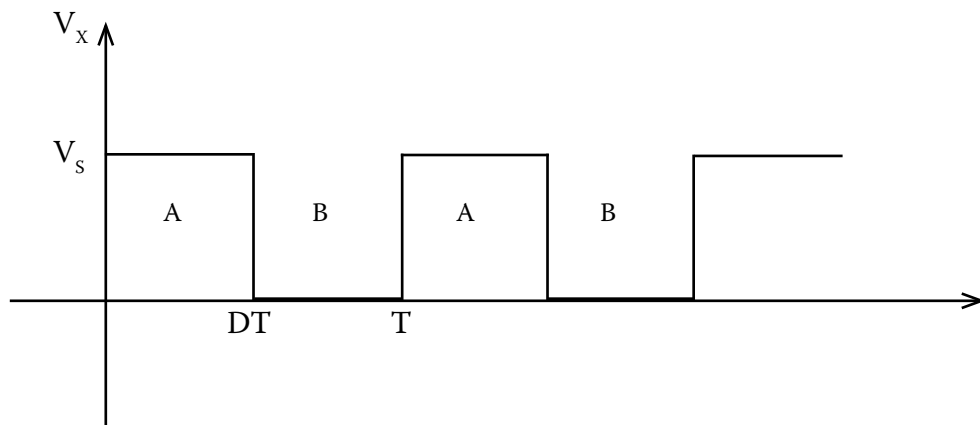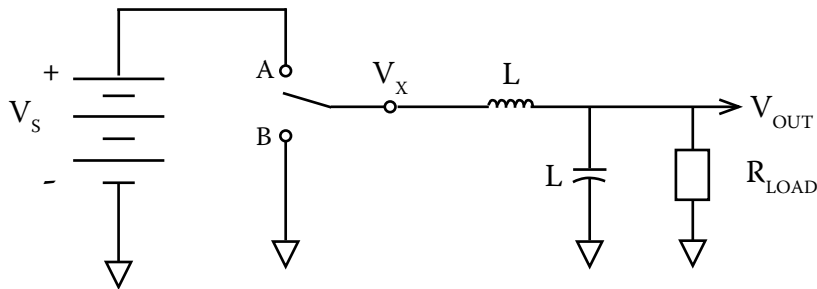Using inductors, capacitors, and switches is in fact how we do efficient power conversion.



6.302 Feedback Systems

Recitation 24: Feedback Applications

Prof. Joel L. Dawson


The inductor and capacitor form a low-pass filter, allowing us to extract the DC value of V_x .

$$1) \quad V_x = DV_s$$

$$2) \quad V_o = \frac{1}{s^2LC + s^{L/R} + 1} V_x$$

$$\hookrightarrow V_o = \frac{V_s}{s^2LC + s^{L/R} + 1} \cdot D$$

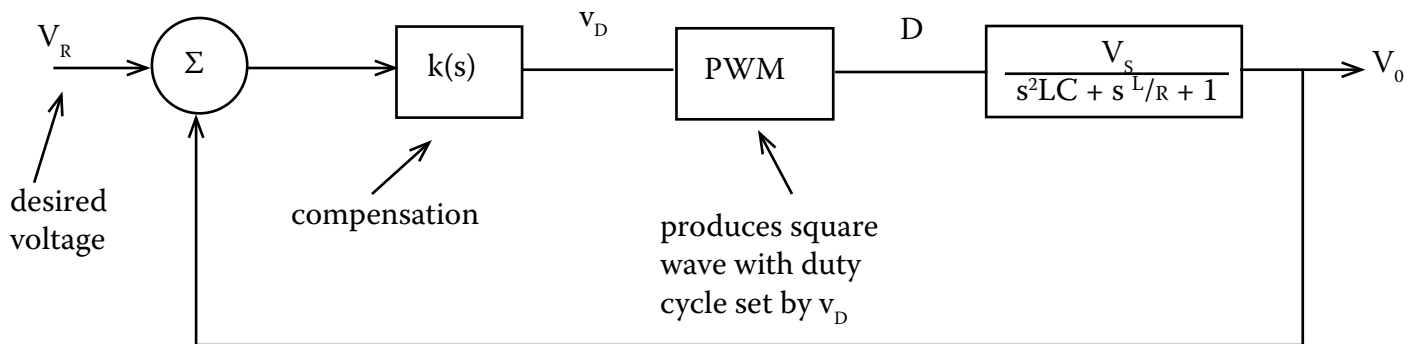So if we have a way of generating a variable-duty-cycle square wave, a feedback switching power converter might look something like this:



This is a very efficient way to generate voltages from a fixed supply.

\hookrightarrow It is also yet another system that feedback theory helps us design.