


# 6.302 Feedback Systems

Recitation 5: Op-amp Circuits and Analog Computers

Prof. Joel L. Dawson

In lecture, Prof. Roberge spoke of building elaborate systems using op-amp circuits. When we do this, we habitually make statements like, "...and we'll choose the dynamics such that the poles contributed by the op-amps themselves are negligible." Let's discuss.

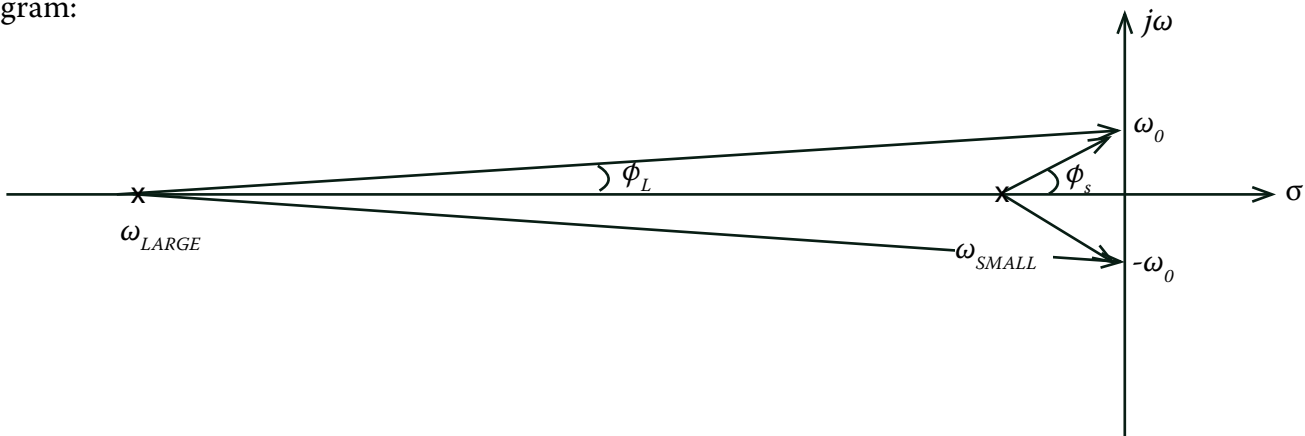Consider a two-pole system whose behavior interests us only in the range from DC to  $\omega_0$ . A pole-zero diagram:



The angle  $\phi_L$  is small compared to  $\phi_s$ . => pole @  $\omega_{LARGE}$  contributes very little phase shift.

For the frequency response evaluated at  $s=j\omega_0$ :

$$\frac{1}{\left(\frac{s}{\omega_L} + 1\right) \left(\frac{s}{\omega_S} + 1\right)} \Bigg|_{s=j\omega_0} = \frac{1}{\left(\frac{j\omega_0}{\omega_L} + 1\right) \left(\frac{j\omega_0}{\omega_S} + 1\right)}$$

$$\frac{\omega_0}{\omega_L} \ll 1, \quad \frac{\omega_0}{\omega_S} \text{ is on the order of unity (at least)!}$$


So this transfer function is well-approximated by the single-pole transfer function  $\frac{1}{\left(\frac{s}{\omega_S} + 1\right)}$  for frequencies from DC to  $\omega_0$ .

# 6.302 Feedback Systems

Recitation 5: Op-amp Circuits and Analog Computers

Prof. Joel L. Dawson

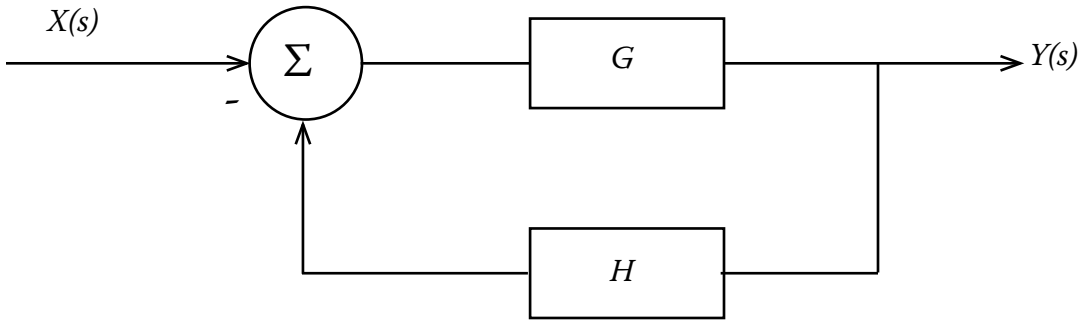But what determines  $\omega_o$ ? Depends on the context, but for feedback systems we often look at the loop transmission.




When  $|L(s)| = |GH| \ll 1$ , we arguably have an open-loop system:

$$\frac{Y(s)}{X(s)} = \frac{G}{1+GH} \approx G$$

So when we're looking for dynamics to ignore, we will often discard poles that are large compared to the loop crossover frequency, or the frequency at which  $|L(S)| = 1$ .
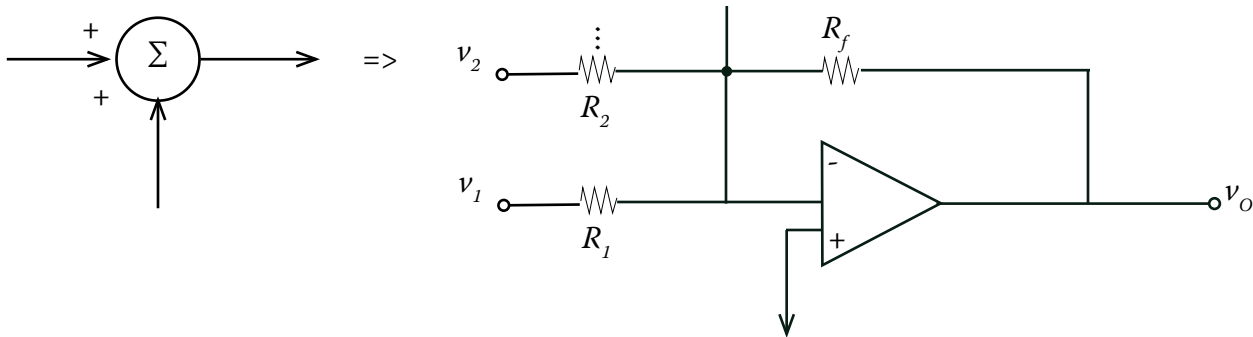
## Op-amp circuits for modeling our systems

We need an integrator, a summer, an inversion, and a gain.




$$V_o = -\frac{R_f}{R_1} V_1 + \left(-\frac{R_f}{R_2}\right) V_2 + \dots$$


# 6.302 Feedback Systems

Recitation 5: Op-amp Circuits and Analog Computers


Prof. Joel L. Dawson

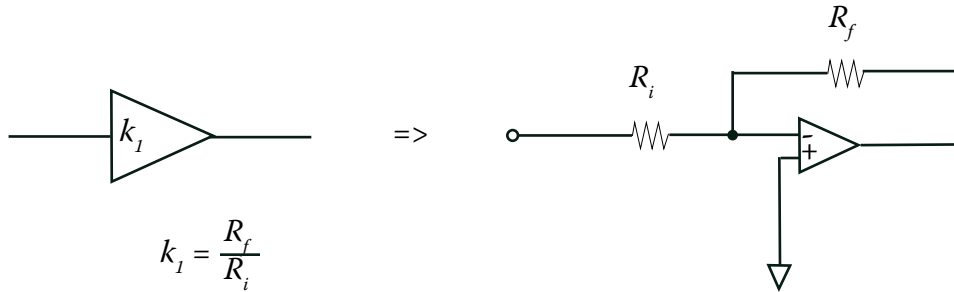

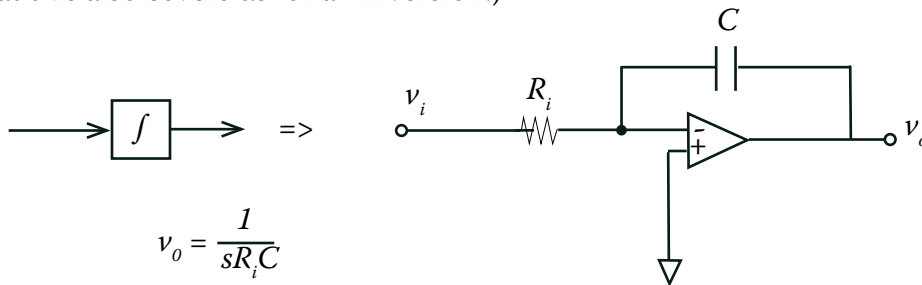
(Note that this also covers us for an inversion.)



And, a block that we do not use:

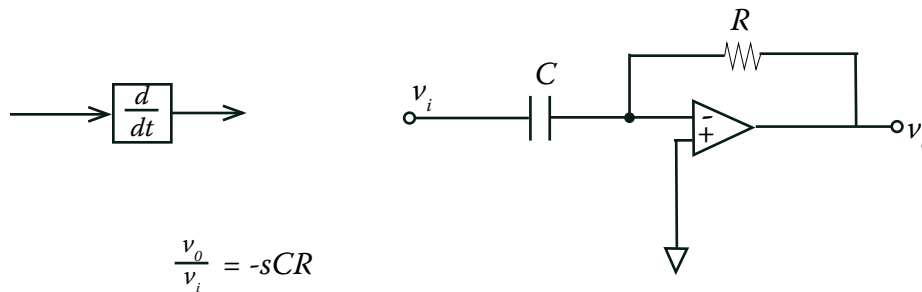

Difficult to manage in a noisy world:

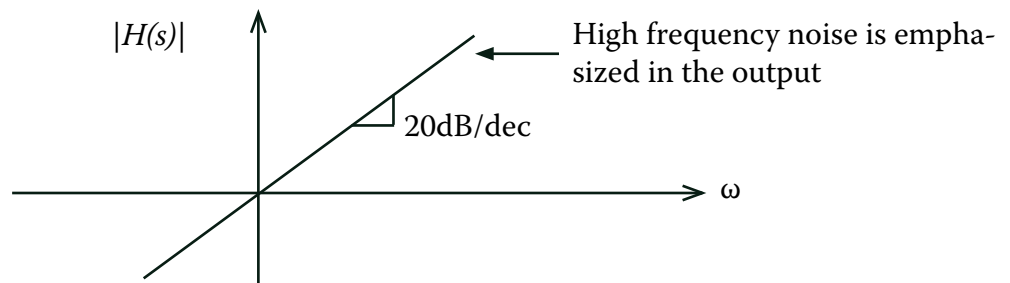

# 6.302 Feedback Systems

Recitation 5: Op-amp Circuits and Analog Computers

Prof. Joel L. Dawson

Also against the differentiator: it's hard enough to get high gain at DC. High gain at high frequencies? Forget it.

Now, on to building analog computers. Suppose we have an all-pole system. It begins as a differential equation:

$$a_n \frac{d^n y}{dt^n} + a_{n-1} \frac{d^{n-1} y}{dt^{n-1}} + a_{n-2} \frac{d^{n-2} y}{dt^{n-2}} + \dots + a_0 y = x$$

Completely general procedure starts with taking the Laplace transform:

$$(a_n s^n + a_{n-1} s^{n-1} + a_{n-2} s^{n-2} + \dots + a_0) Y(s) = x(s)$$


$$\left[ \text{The system function, BTW, is: } \frac{Y(s)}{x(s)} = \frac{1}{a_n s^n + a_{n-1} s^{n-1} + a_{n-2} s^{n-2} + \dots + a_0} \right]$$

Solve for the highest order derivative:

$$a_n s^n Y(s) = X(s) - (a_{n-1} s^{n-1} + a_{n-2} s^{n-2} + \dots + a_0) Y(s)$$

$$s^n Y(s) = \frac{1}{a_n} X(s) - \left[ \frac{a_{n-1}}{a_n} s^{n-1} + \frac{a_{n-2}}{a_n} s^{n-2} + \dots + \frac{a_0}{a_n} \right] Y(s)$$

Put down a big summing junction:

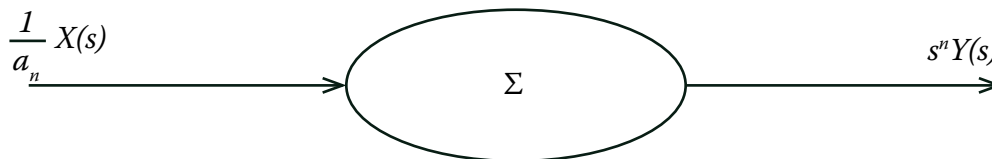


# 6.302 Feedback Systems


Recitation 5: Op-amp Circuits and Analog Computers

Prof. Joel L. Dawson

Generate the derivatives that you need:

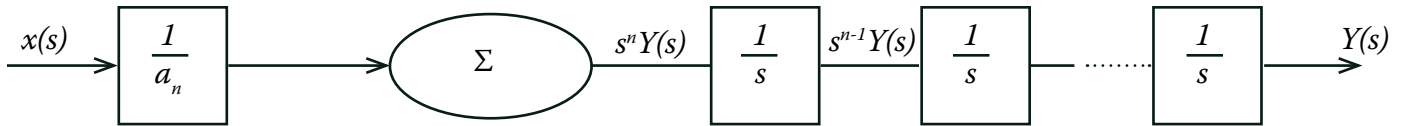

Complete the mapping:

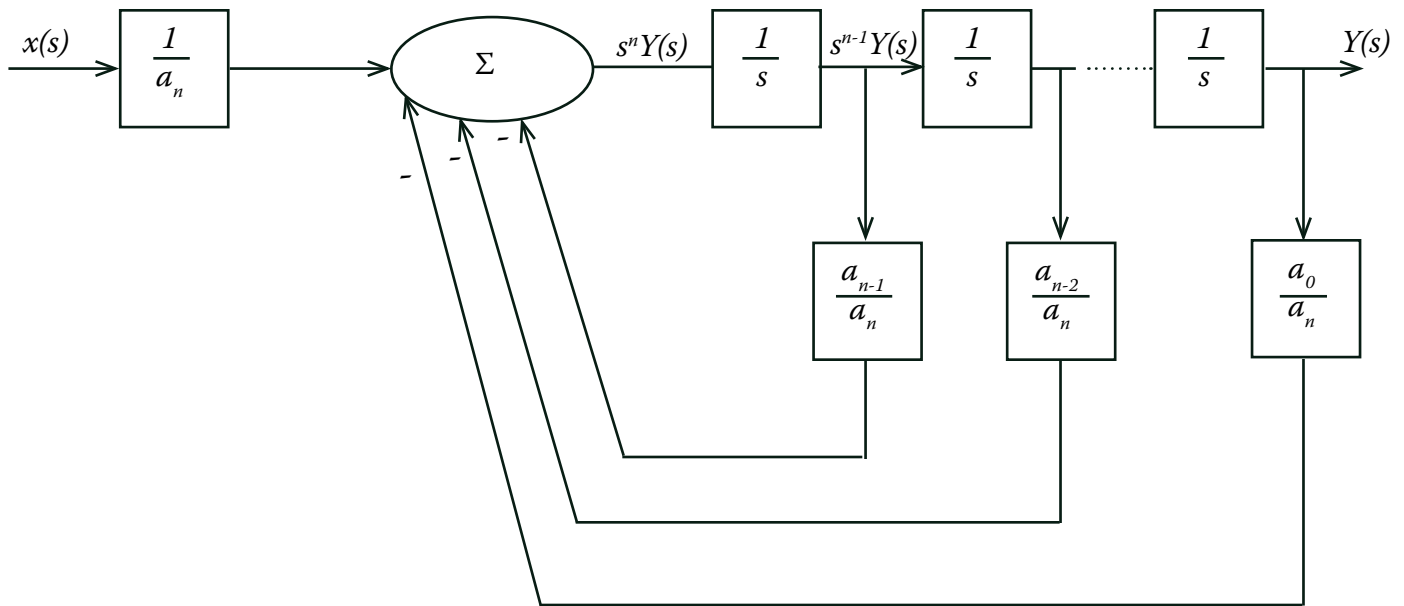

EXAMPLE: First order system

$$\frac{Y(s)}{x(s)} = \frac{1}{\tau s + 1}$$

$$\hookrightarrow (\tau s + 1)Y(s) = x(s)$$


$$sY(s) = \frac{1}{\tau} x(s) - \frac{1}{\tau} Y(s)$$

=>

# 6.302 Feedback Systems


Recitation 5: Op-amp Circuits and Analog Computers

Prof. Joel L. Dawson

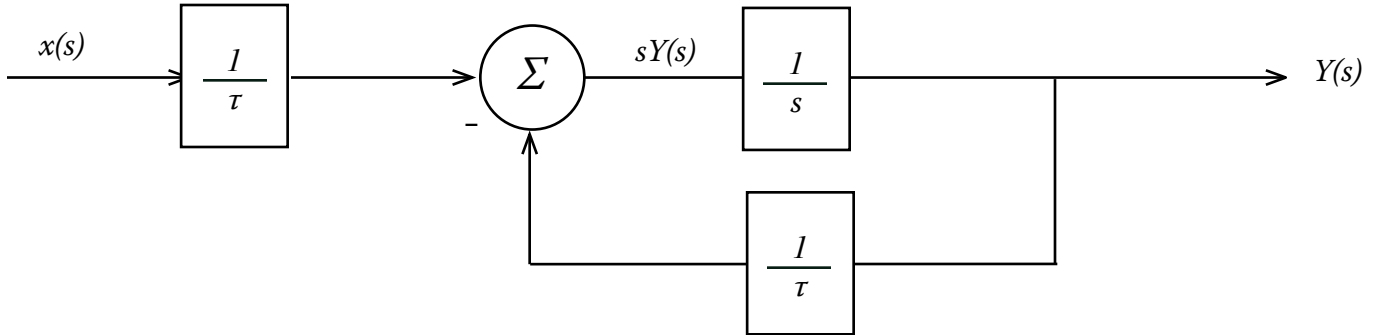


2nd order system from class: 
$$\frac{v_o}{v_i} = \frac{1}{\frac{s^2}{\omega_n^2} + \frac{2\zeta s}{\omega_n} + 1}$$

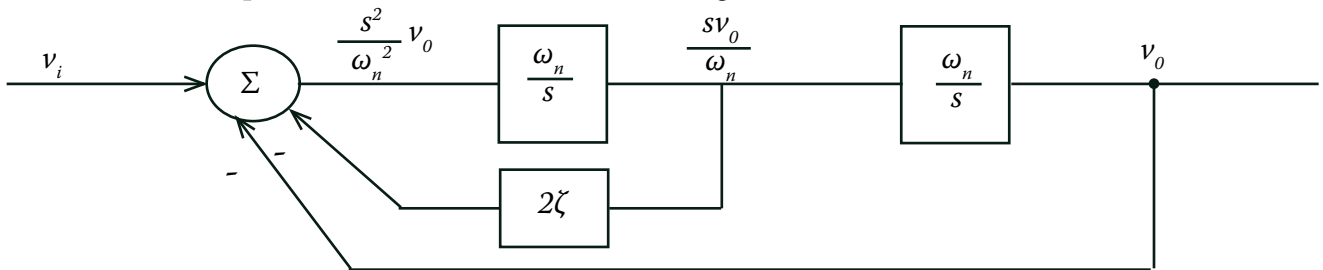
With a little bit of manipulation, we can write the block diagram as



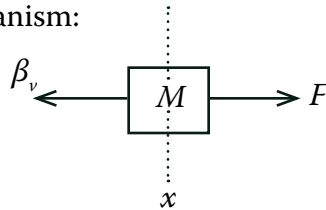If we built this as an electronic circuit, it would be analogous to our mechanical system consisting of a mass, a viscous fluid, and a forcing mechanism:



Is the position where I want it?

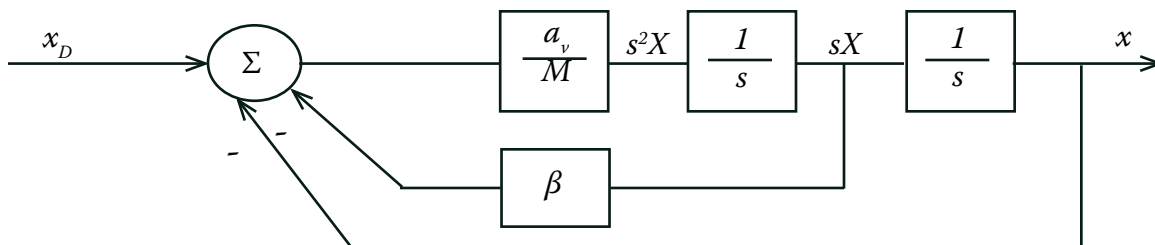


# 6.302 Feedback Systems

Recitation 5: Op-amp Circuits and Analog Computers

Prof. Joel L. Dawson

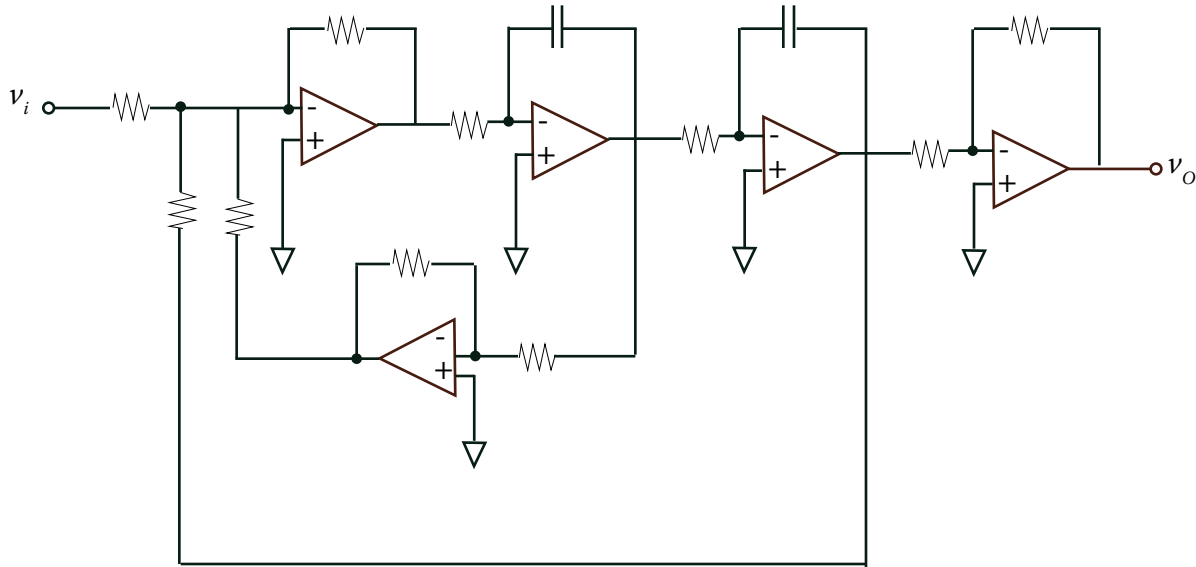An analog computer might look something like this:



Make sure that  $\omega_n$  is small compared to the parasitic poles of the op-amps. Then, we get a very good analog.